#### Lab 5

## Verilog code- top module

```
module top(
  input clk,
  input [3:0] a,
  input [3:0] b,
  output [7:0] cathode,
  output [3:0] anode
  );
  wire [7:0] num;
  wire [3:0] thousands;
  wire [3:0] hundreds;
  wire [3:0] tens;
  wire [3:0] ones;
  mul_4x4 fun1(.x(a),.y(b),.pro(num));
  bin2bcd
fun2(.number(num),.thousands(thousands),.hundreds(hundreds),.tens(tens),.ones(ones));
  sevenseg
fun3(.clk(clk),.ones(ones),.tens(tens),.hundreds(hundreds),.thousands(thousands),.anode(anod
e),.cathode(cathode));
endmodule
```

# Verilog code- seven segment display

```
// input [3:0] num,
  output [7:0] cathode,
  output [3:0] anode
  );
  reg [6:0]sseg temp;
   reg [3:0]an_temp = 4'b1110;
   reg [17:0] count; //the 18 bit counter which allows us to multiplex at 1000Hz
   always @ (posedge clk)
   begin
    count <= count + 1;
   end
       //code for display multiple digits (do not initialize an_temp in line 41 and comment out
lines 44 to 60)
   always @ (*)
   begin
    case(count[17:16]) //using only the 2 MSB's of the counter
     2'b00: //When the 2 MSB's are 00 enable the fourth display
     begin
      case(ones)
         4'd0 : sseg_temp = 7'b0000001; //to display 0
         4'd1 : sseg_temp = 7'b1001111; //to display 1
         4'd2 : sseg_temp = 7'b0010010; //to display 2
         4'd3: sseg_temp = 7'b0000110; //to display 3
         4'd4: sseg_temp = 7'b1001100; //to display 4
         4'd5 : sseg_temp = 7'b0100100; //to display 5
         4'd6: sseg_temp = 7'b0100000; //to display 6
         4'd7 : sseg_temp = 7'b0001111; //to display 7
         4'd8: sseg_temp = 7'b0000000; //to display 8
         4'd9 : sseg_temp = 7'b0000100; //to display 9
         default : sseg_temp = 7'b1111110; //dash
      endcase
      //sseg = ones;
      an_{temp} = 4'b1110;
     end
     2'b01: //When the 2 MSB's are 01 enable the third display
     begin
        case(tens)
         4'd0 : sseg_temp = 7'b0000001; //to display 0
```

```
4'd1: sseg_temp = 7'b1001111; //to display 1
    4'd2 : sseg_temp = 7'b0010010; //to display 2
    4'd3 : sseg_temp = 7'b0000110; //to display 3
    4'd4: sseg_temp = 7'b1001100; //to display 4
    4'd5 : sseg_temp = 7'b0100100; //to display 5
    4'd6 : sseg_temp = 7'b0100000; //to display 6
    4'd7 : sseg_temp = 7'b0001111; //to display 7
    4'd8: sseg_temp = 7'b0000000; //to display 8
    4'd9: sseg_temp = 7'b0000100; //to display 9
    default : sseg_temp = 7'b1111110; //dash
   endcase
 //sseg = tens;
 an_{temp} = 4'b1101;
end
2'b10: //When the 2 MSB's are 10 enable the second display
begin
 case(hundreds)
    4'd0 : sseg_temp = 7'b0000001; //to display 0
    4'd1: sseg_temp = 7'b1001111; //to display 1
    4'd2 : sseg_temp = 7'b0010010; //to display 2
    4'd3: sseg_temp = 7'b0000110; //to display 3
    4'd4 : sseg_temp = 7'b1001100; //to display 4
    4'd5 : sseg_temp = 7'b0100100; //to display 5
    4'd6: sseg_temp = 7'b0100000; //to display 6
    4'd7: sseg_temp = 7'b0001111; //to display 7
    4'd8 : sseg_temp = 7'b0000000; //to display 8
    4'd9 : sseg_temp = 7'b0000100; //to display 9
    default: sseg_temp = 7'b1111110; //dash
 endcase
 //sseg = hundreds;
 an temp = 4'b1011;
end
2'b11: //When the 2 MSB's are 11 enable the first display
begin
 case(thousands)
    4'd0 : sseg_temp = 7'b0000001; //to display 0
    4'd1: sseg_temp = 7'b1001111; //to display 1
    4'd2 : sseg_temp = 7'b0010010; //to display 2
    4'd3 : sseg_temp = 7'b0000110; //to display 3
```

```
4'd4 : sseg_temp = 7'b1001100; //to display 4
         4'd5 : sseg_temp = 7'b0100100; //to display 5
         4'd6 : sseg_temp = 7'b0100000; //to display 6
         4'd7 : sseg_temp = 7'b0001111; //to display 7
         4'd8: sseg_temp = 7'b0000000; //to display 8
         4'd9 : sseg_temp = 7'b0000100; //to display 9
         default : sseg_temp = 7'b1111110; //dash
     endcase
     //sseg = thousands;
     an_temp = 4'b0111;
    end
   endcase
   end
  assign anode = an_temp;
  assign cathode = {sseg_temp, 1'b1};
endmodule
```

## Verilog code- full adder

```
module full_adder(
input a,
input b,
input c,
output sum,
output carry
);
assign sum=a^b^c;
assign carry=(a & b) | (c&(a^b));
endmodule
```

#### Verilog code- 4x4 multiplier

```
module mul_4x4(
```

```
input [3:0] x,
input [3:0] y,
output [7:0] pro
);
wire c1,c2,c3,c4,c5,c6,c7,c8,c9,c10,c11,c12;
wire sum1,sum2,sum3,sum4,sum5,sum6;
assign pro[0]=x[0] & y[0];
full_adder fun1(.a(y[0]&x[1]),.b(y[1]&x[0]),.c(1'b0),.sum(pro[1]),.carry(c1));
full_adder fun2(.a(y[0]&x[2]),.b(y[1]&x[1]),.c(c1),.sum(sum1),.carry(c2));
full_adder fun3(.a(y[2]&x[0]),.b(sum1),.c(1'b0),.sum(pro[2]),.carry(c3));
full_adder fun4(.a(y[0]&x[3]),.b(y[1]&x[2]),.c(c2),.sum(sum2),.carry(c4));
full_adder fun5(.a(c3),.b(y[2]&x[1]),.c(sum2),.sum(sum3),.carry(c5));
full_adder fun6(.a(y[3]&x[0]),.b(1'b0),.c(sum3),.sum(pro[3]),.carry(c6));
full_adder fun7(.a(y[1]&x[3]),.b(1'b0),.c(c4),.sum(sum4),.carry(c7));
full_adder fun8(.a(sum4),.b(y[2]&x[2]),.c(c5),.sum(sum5),.carry(c8));
full_adder fun9(.a(y[3]&x[1]),.b(sum5),.c(c6),.sum(pro[4]),.carry(c9));
full adder fun10(.a(y[2]&x[3]),.b(c8),.c(c7),.sum(sum6),.carry(c10));
full_adder fun11(.a(y[3]&x[2]),.b(sum6),.c(c9),.sum(pro[5]),.carry(c11));
full_adder fun12(.a(y[3]&x[3]),.b(c11),.c(c10),.sum(pro[6]),.carry(c12));
assign pro[7]=c12;
```

endmodule

## Verilog code- binary to bcd

```
`timescale 1ns / 1ps
//below Binary to BCD is taken from the following link:
http://www.deathbylogic.com/2013/12/binary-to-binary-coded-decimal-bcd-converter/
module bin2bcd(number, thousands, hundreds, tens, ones);
```

```
// I/O Signal Definitions
input [7:0] number;
output reg [3:0] thousands;
output reg [3:0] hundreds;
output reg [3:0] tens;
output reg [3:0] ones;
// Internal variable for storing bits
reg [19:0] shift;
integer i;
always @(number)
begin
  // Clear previous number and store new number in shift register
  shift[19:8] = 0;
  shift[7:0] = number;
  // Loop eight times
  for (i=0; i<8; i=i+1) begin
   if (shift[11:8] >= 5)
     shift[11:8] = shift[11:8] + 3;
   if (shift[15:12] >= 5)
      shift[15:12] = shift[15:12] + 3;
   if (shift[19:16] >= 5)
     shift[19:16] = shift[19:16] + 3;
   // Shift entire register left once
   shift = shift << 1;
  end
  // Push decimal numbers to output
  hundreds = shift[19:16];
  tens
        = shift[15:12];
  ones = shift[11:8];
  thousands= 4'b0000;
end
```


endmodule

#### **XDC** file


```
# Clock signal
set_property PACKAGE_PIN W5 [get_ports clk]
      set_property IOSTANDARD LVCMOS33 [get_ports clk]
# Switches
set_property PACKAGE_PIN V17 [get_ports {a[0]}]
      set_property IOSTANDARD LVCMOS33 [get_ports {a[0]}]
set_property PACKAGE_PIN V16 [get_ports {a[1]}]
      set_property IOSTANDARD LVCMOS33 [get_ports {a[1]}]
set_property PACKAGE_PIN W16 [get_ports {a[2]}]
      set_property IOSTANDARD LVCMOS33 [get_ports {a[2]}]
set property PACKAGE PIN W17 [get ports {a[3]}]
      set property IOSTANDARD LVCMOS33 [get_ports {a[3]}]
set_property PACKAGE_PIN W15 [get_ports {b[0]}]
      set_property IOSTANDARD LVCMOS33 [get_ports {b[0]}]
set_property PACKAGE_PIN V15 [get_ports {b[1]}]
      set property IOSTANDARD LVCMOS33 [get_ports {b[1]}]
set_property PACKAGE_PIN W14 [get_ports {b[2]}]
      set_property IOSTANDARD LVCMOS33 [get_ports {b[2]}]
set property PACKAGE PIN W13 [get ports {b[3]}]
      set_property IOSTANDARD LVCMOS33 [get_ports {b[3]}]
#7 segment display
set property PACKAGE PIN W7 [get ports {cathode[7]}]
  set_property IOSTANDARD LVCMOS33 [get_ports {cathode[7]}]
set_property PACKAGE_PIN W6 [get_ports {cathode[6]}]
  set_property IOSTANDARD LVCMOS33 [get_ports {cathode[6]}]
set_property PACKAGE_PIN U8 [get_ports {cathode[5]}]
  set_property IOSTANDARD LVCMOS33 [get_ports {cathode[5]}]
set_property PACKAGE_PIN V8 [get_ports {cathode[4]}]
  set property IOSTANDARD LVCMOS33 [get_ports {cathode[4]}]
set_property PACKAGE_PIN U5 [get_ports {cathode[3]}]
  set_property IOSTANDARD LVCMOS33 [get_ports {cathode[3]}]
set_property PACKAGE_PIN V5 [get_ports {cathode[2]}]
  set property IOSTANDARD LVCMOS33 [get_ports {cathode[2]}]
set_property PACKAGE_PIN U7 [get_ports {cathode[1]}]
  set_property IOSTANDARD LVCMOS33 [get_ports {cathode[1]}]
set_property PACKAGE_PIN V7 [get_ports cathode[0]]
  set_property IOSTANDARD LVCMOS33 [get_ports cathode[0]]
```

```
set_property PACKAGE_PIN U2 [get_ports {anode[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[0]}]
set_property PACKAGE_PIN U4 [get_ports {anode[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[1]}]
set_property PACKAGE_PIN V4 [get_ports {anode[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[2]}]
set_property PACKAGE_PIN W4 [get_ports {anode[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[3]}]
```

#### **Outputs**

 

A= 15 B= 15 Product= 225 (num)

 

A= 15 B= 13 Product= 195 (num)